

6.013 Final project Report

Andres Erbsen, Justin Graves, Dimitris Koutentakis

May 14, 2017

Contents

1	Introduction	2
2	Filter Design	2
2.1	Short-short half wave resonator	2
2.2	Short-short 2.4 GHz resonator	2
2.3	Single stub band-stop filter	2
2.4	multiple stub band-pass filter	2
3	Measurements	3
4	Discussion	3

1 Introduction

2 Filter Design

In order to design our filters, we had to apply some of the basic knowledge we acquired in the lectures towards the end of the semester. More specifically, we had to apply knowledge regarding transmission line resonators as well as smith charts and stubs.

By calculating the dimensions for our given substrate and target frequencies we were able to build the filters desired. The filters that we ended up building are:

- A short-short half wave resonator for $\lambda = ?$,
- A short-short half wave resonator for $f = 2.4GHz$,
- A single stub band-stop resonator, and
- A multiple stub band pass approximation filter

2.1 Short-short half wave resonator

For the first short-short half-wave resonator, we used the dimensions of the original board given. More specifically, we used a length of $D = ?$ and δ very small in order to maximize our Q .

$$D =$$

2.2 Short-short 2.4 GHz resonator

describe

2.3 Single stub band-stop filter

describe

2.4 multiple stub band-pass filter

describes

3 Measurements

describe

4 Discussion

describe